

BCA-03

June - Examination 2016

BCA Pt. I Examination**Basic Electronics****Paper - BCA-03****Time : 3 Hours]****[Max. Marks :- 100**

Note: The question paper is divided into three sections A, B and C. Write answers as per given instructions.

Section - A**10 × 2 = 20**

(Very Short Answer Questions)

Note: Answer **all** questions. As per the nature of the question delimit your answer in one word, one sentence or maximum upto 30 words. Each question carries 2 marks.

- 1) (i) Write the statement of Kirchoff's Current Law.
- (ii) What is biasing process in semiconductors?
- (iii) What is diffusion?
- (iv) What is edge triggering in digital?
- (v) What is flip flop in digital?
- (vi) What is duality property in digital?
- (vii) What is inductance?
- (viii) What are the latches in digital?

- (ix) Define rectification.
- (x) Which kind of device is FET?

Section - B**4 × 10 = 40**

(Short Answer Questions)

Note: Answer **any four** questions. Each answer should not exceed 200 words. Each question carries 10 marks.

- 2) Describe the wiring system with suitable diagram.
- 3) Describe differences between CB CE and CC configuration of BJT.
- 4) Describe diode as a switch.
- 5) Explain briefly clipper and clamper applications of diode with any example.
- 6) Describe T-flip flop with state table and state diagram.
- 7) Describe Thevenin's theorem of circuit analysis.
- 8) Describe all possible combinations of Boolean algebra.
- 9) Explain briefly the Earthing principle.

Section - C**2 × 20 = 40**

(Long Answer Questions)

Note: Answer **any two** questions. You have to delimit your each answer maximum upto 500 words. Each question carries 20 marks.

- 10) What do you mean by Race condition? Explain the working of JK flip flop with the help of symbolic diagram.
- 11) Explain 4-bit synchronous counter with their timing diagram and operation.
- 12) What do you mean by rectifiers? Also explain its working.
- 13) Explain intrinsic and extrinsic semiconductors.
