

MCA-02
June - Examination 2016
MCA 1st Year Examination
Digital Logic
Paper - MCA-02

Time : 3 Hours]

[Max. Marks :- 80

Note: The question paper is divided into three sections A, B and C. Write answers as per given instructions.

Section - A

8 × 2 = 16

(Very Short Answer Questions)

Note: Answer **all** questions. As per the nature of the question delimit your answer in one word, one sentence or maximum upto 30 words. Each question carries 2 marks.

- 1) (i) What is use of fixed point representation?
- (ii) What is statement of duality property?
- (iii) What is full form of ASCII?
- (iv) What is SRAM?
- (v) Write any two types of decimal to binary conversions?
- (vi) What is the flow of BCD?
- (vii) Write any two benefits of shift registers?
- (viii) What is ROM?

Section - B**4 × 8 = 32**

(Short Answer Questions)

Note: Answer **any four** questions. Each answer should not exceed 200 words. Each question carries 8 marks.

- 2) Discuss the basic 2-input Multiplexer.
- 3) How data distributors work?
- 4) Discuss decimal to BCD encoder.
- 5) Simplify the following Boolean expression:
$$F = ABC + AB'CD' + A'C' + BCD'$$
- 6) Discuss serial-in-parallel out register.
- 7) Describe T flip flop with suitable diagram and functionality.
- 8) Describe half subtractor and full subtractor with diagram and truth tables.
- 9) Explain the universal gate property of NOR gate for XOR, OR gate formation?

Section - C**2 × 16 = 32**

(Long Answer Questions)

Note: Answer **any two** questions. You have to delimit your each answer maximum upto 500 words. Each question carries 16 marks.

- 10) Design a 4-bit Parallel-in-serial-out shift register with neat sketch.
 - 11) Explain the working and detailed classification of serial to parallel converter.
 - 12) Write a short note on:
 - a) Encoders
 - b) Applications of shift registers
 - 13) Explain the working and basic structure of DRAM.
-