

BCA-03

December - Examination 2015

B.C.A. Ist Year Examination**Basic Electronics****Paper - BCA-03****Time : 3 Hours]****[Max. Marks :- 100**

Note: The question paper is divided into three sections A, B and C. Write answers as per given instructions.

Section - A

10 x 2 = 20

(Very Short Answer Questions)

Note: Answer all questions. As per the nature of the question delimit your answer in one word, one sentence or maximum up to 30 words. Each question carries 2 marks.

- 1) (i) Write the statement of Kirchhoff's voltage law.
- (ii) What is doping process in semiconductors?
- (iii) What is drift current?
- (iv) What is level triggering in digital?
- (v) What is working of D- flip flop?
- (vi) What is SOP and POS terms in Boolean algebra?
- (vii) What is capacitance?

- (viii) What are the registers in digital?
- (ix) What is asynchronous counter?
- (x) Which kind of device is transistor?

Section - B

4 x 10 = 40

(Short Answer Questions)

Note: Answer any four questions. Each answer should not exceed 200 words. Each question carries 10 marks.

- 2) Describe the importance of copper wiring system suitable for circuits.
- 3) Describe differences between NPN and PNP BJT.
- 4) Describe transistor as a switch.
- 5) Explain briefly amplifiers as an application of transistor with any example.
- 6) Describe D- flip flop with state table and state diagram.
- 7) Describe Norton's theorem of circuit analysis.
- 8) Describe duality property of Boolean algebra.
- 9) Explain briefly the power supply installation principle.

Section - C

2 x 20 = 40

(Long Answer Questions)

Note: Answer any two questions. You have to delimit your answer maximum up to 500 words. Each question carries 20 marks.

- 10) Explain edge triggered R-S flip flop with helping of symbolic diagram and its operations.
 - 11) Explain 4-bit asynchronous counter with their timing diagram and operation.
 - 12) Explain full wave rectifier and their working.
 - 13) Explain CE configuration with neat sketches of input and output characteristics curves.
- _____