

BCA-03

December - Examination 2016

BCA Pt. I Examination**Basic Electronics****Paper - BCA-03****Time : 3 Hours]****[Max. Marks :- 100**

Note: The question paper is divided into three sections A, B and C. Write answers as per given instructions.

Section - A**10 × 2 = 20**

(Very Short Answer Questions)

Note: Answer **all** questions. As per the nature of the question delimit your answer in one word, one sentence or maximum upto 30 words. Each question carries 2 marks.

- 1) (i) Write the statement of Kirchhoff's Voltage Law.
- (ii) What is drift current?
- (iii) What is transistor?
- (iv) What is work of zener diode?
- (v) Write about ripple factor.
- (vi) What is Boolean algebra?
- (vii) Write about logic gates.
- (viii) What do you understand by Universal Gate?

- (ix) What do you mean by UJT?
- (x) What do you understand by latches?

Section - B**4 × 10 = 40**

(Short Answer Questions)

Note: Answer **any four** questions. Each answer should not exceed 200 words. Each question carries 10 marks.

- 2) Discuss the half wave rectifier using crystal diode.
- 3) Explain Thevenin's theorem of circuit analysis.
- 4) Discuss RS flip flop with state table and state diagram.
- 5) Explain the early effect in transistors.
- 6) Discuss SOP and POS process of K-MAP briefly.
- 7) Describe the importance of load line analysis.
- 8) Describe CMOs, NMOS, and PMOS.
- 9) Explain the working of CE amplifier.

Section - C**2 × 20 = 40**

(Long Answer Questions)

Note: Answer **any two** questions. You have to delimit your answer maximum upto 500 words. Each question carries 20 marks.

- 10) Explain Intrinsic and Extrinsic semiconductors in details.
 - 11) Explain clipper and clamper applications of diode with examples briefly.
 - 12) Explain construction and characteristics of P-channel MOSFET with neat and clean diagram, also define threshold voltage.
 - 13) Explain 4 bit Asynchronous counter with their timing diagram and operations.
-