

**BCA-03**

December - Examination 2017

**BCA Pt. I Examination****Basic Electronics****Paper - BCA-03****Time : 3 Hours ]****[ Max. Marks :- 100**

**Note:** The question paper is divided into three sections A, B and C. Write answers as per given instructions.

**Section - A****10 × 2 = 20**

(Very Short Answer Questions)

**Note:** Answer **all** questions. As per the nature of the question delimit your answer in one word, one sentence or maximum upto 30 words. Each question carries 2 marks.

- 1) (i) What is diffusion current?
- (ii) What is basic use of zener diode?
- (iii) Which kind of device is Transistor?
- (iv) What is latch in digital electronics?
- (v) What do you understand by Early Effect in Transistors?
- (vi) What is flip flop?

- (vii) Write any two benefits of designing Universal Gates?
- (viii) What do you mean by doping concentration?
- (ix) Write the statement of Fermi Dirac Energy function.
- (x) Write about tunnel breakdown.

**Section - B****4 × 10 = 40**

(Short Answer Questions)

**Note:** Answer **any four** questions. Each answer should not exceed 200 words. Each question carries 10 marks.

- 2) Discuss the functioning of Full Wave Rectifier.
- 3) Explain stabilizing factor?
- 4) Discuss the CC configuration of amplifier with neat and clean diagram.
- 5) Describe minimization through K-Map for  $F=ABCD+A'B'C'D'$ .
- 6) Explain the differences CMOS, NMOS, PMOS and TTL.
- 7) Describe statement of duality property with an example.
- 8) Describe the conversion of OR, EX-OR operations by using NAND Gate with the property of Universal Gate.
- 9) Explain current characteristics in PNP transistor.

**Section - C****2 × 20 = 40**

(Long Answer Questions)

**Note:** Answer **any two** questions. You have to delimit your each answer maximum upto 500 words. Each question carries 20 marks.

- 10) Describe the functioning of Zener diode in line and load characteristics.
- 11) Explain the various series and shunt biasing operations of clipper and clamper circuit.
- 12) Explain SOP and POS process of K-map.
- 13) Explain Donor and Acceptor Concentration phenomenon in intrinsic and extrinsic semiconductors.