BCA-03

June - Examination 2017

BCA Pt. I Examination

Basic Electronics

Paper - BCA-03

Time : 3 Hours]

[Max. Marks :- 100

Note: The question paper is divided into three sections A, B and C. Write answers as per given instructions.

Section - A

 $10 \times 2 = 20$

(Very Short Answer Questions)

- **Note:** Answer **all** questions. As per the nature of the question delimit your answer in one word, one sentence or maximum up to 30 words. Each question carries 2 marks.
- 1) (i) What is the requirement of Boolean algebra ?
 - (ii) What is the use of load line ?
 - (iii) What is the property of demorgen's theorem ?
 - (iv) What is full form of POS ?
 - (v) What is Biasing ?
 - (vi) What is Donor concentration in semiconductors ?
 - (vii) What is property of ideal diode ?

285

- (viii) Which type of device is diode ?
- (ix) Write any two acceptor atoms name.
- (x) Write Pauli Exclusion rule.

Section - B

 $4 \times 10 = 40$

(Short Answer Questions)

- **Note:** Answer **any four** questions. Each answer should not exceed 200 words. Each question carries 10 marks.
- 2) Discuss the effect of various types of breakdown regions.
- 3) Discuss the working of CB amplifier.
- 4) Discuss why collector current is less than emitter current ?
- 5) Explain role of early effect in transistors.
- 6) Discuss the working of half wave rectifier using crystal diode.
- 7) Describe AC and DC resistances of crystal diodes.
- 8) Describe the designing of CMOS devices and their use.
- 9) Explain Fermi Dirac energy function of semiconductors.

Section - C

(Long Answer Questions)

- **Note:** Answer **any two** questions. You have to delimit your each answer maximum up to 500 words. Each question carries 20 marks.
- 10) Explain various type of Electrical Wiring according to their use.
- 11) Draw the AND GATE, NAND GATE and EX-OR GATE using NOR GATE.
- 12) Explain various types of Series and Shunt biasing operations of Clamper diode circuit.
- 13) Explain current characteristics of PNP transistor and also discuss the leakage current behaviour.