

BCA-03

June - Examination 2018

BCA Pt. I Examination**Basic Electronics****Paper - BCA-03****Time : 3 Hours]****[Max. Marks :- 100**

Note: The question paper is divided into three sections A, B and C. Write answers as per the given instructions.

Section - A**10 × 2 = 20**

(Very Short Answer Type Questions)

Note: Answer **all** questions. As per the nature of the question delimit your answer in one word, one sentence or maximum up to 30 words. Each question carries 2 marks.

- 1) (i) Write about Stability and Causality?
- (ii) What is diffusion current?
- (iii) Define the term doping concentration?
- (iv) What are SOP and POS terms in digital electronics?
- (v) What is thermal stability in transistors?
- (vi) What is use of clipper and clamper circuits?
- (vii) Define the statement of Fermi-Dirac Statistics?

- (viii) What is mobility and conductivity?
- (ix) What is the work of shift registers?
- (x) What is statement of Thevenin's theorem?

Section - B**4 × 10 = 40**

(Short Answer Questions)

Note: Answer **any four** questions. Each answer should not exceed 200 words. Each question carries 10 marks.

- 2) Discuss the transistor as a switch with its diagram.
- 3) Explain the CE configuration of amplifier with neat and clean diagram.
- 4) Explain NAND Gate operation using NOR Gate and NOR Gate operation using NAND Gate with the property of Universal Gate.
- 5) Describe the functioning of current characteristics in NPN transistor.
- 6) Explain the minimization through K-Map for term $F = ABC + A'B'C + ABC' + A'BC'$.
- 7) Describe CMOS technique with neat and clean diagram with its advantages in electronics.
- 8) Describe all kind of breakdown voltage regions with their suitability of appearance in V-I Characteristics graph
- 9) What do you mean by early effect in transistors?

Section - C**2 × 20 = 40**

(Long Answer Questions)

Note: Answer **any two** questions. You have to delimit your each answer maximum up to 500 words. Each question carries 20 marks.

- 10) Describe the Intrinsic and Extrinsic semiconductors with neat and clean diagram.
 - 11) Design J-K flip flop using R-S flip flop.
 - 12) Explain functioning of Ripple counter with an example.
 - 13) Explain the Norton's theorem with an example.
-